

INTRODUCTION TO COMPUTER TECHNOLOGIES
Arithmetic Circuits PRETEST

- 1) The most significant bit of the binary number 100000 is _____.
- 2) What is the sum of the binary numbers 1111 and 0011? _____
- 3) What is the difference between the binary numbers 1110110 and 1010? _____
- 4) The binary numbers 1110110 equals _____ in decimal?
- 5) A half-adder contains a(n) _____ and a(n) _____ gate.
- 6) A full-adder contains two _____ circuits.
- 7) A full-adder has _____ inputs and _____ outputs.
- 8) A 4-bit parallel adder requires _____.
- 9) _____ additional _____ gate(s) are required to convert a half-adder into a half-subtractor.
- 10) Full-adder and Full-subtractor are classified as _____ circuits.

Refer to Fig. 1 (below) for questions 11 - 16.

 


Figure 1

- 11) The sum output from the full-adder circuit for problem a will be _____ (1 bit).
- 12) The C_o output from the full-adder circuit for problem a will be _____ (1 bit).
- 13) The sum output from the full-adder circuit for problem b will be _____ (1 bit).
- 14) The C_o output from the full-adder circuit for problem b will be _____ (1 bit).
- 15) The sum output from the full-adder circuit for problem c will be _____ (1 bit).
- 16) The C_o output from the full-adder circuit for problem c will be _____ (1 bit).

Refer to Fig. 2 (below) for questions 17 - 25.

Figure 2

- 17) When this unit is adding 1001 to 0101, the control must be _____.
- 18) When this unit is adding 1001 to 0101, the output sum appears as binary _____ (4 bits).
- 19) When this unit is adding 1001 to 0101, the C_{in} input to the full-adder is _____ owing to the disabled AND gate
- 20) The XOR gates function as _____ gates when the control is high (unit in subtract mode).
- 21) When this unit is in subtract mode, the _____ end-around carry technique is used to allow the adders to perform binary subtraction.
- 22) When this unit is subtracting 1010 from 1100, the bits appearing at the B inputs to the full adders will be _____ [4 bits , with the 8s bit on the left and the 1s bit on the right].
- 23) When this unit is subtracting 1010 from 1100, the difference appearing at the output will be binary _____ [4 bits].
- 24) When this unit is subtracting 1010 from 1100, the end-around carry line will be _____ (HIGH, LOW).
- 25) This unit can be best described as a(n) _____ adder/subtractor.
- 26) What is the binary product of 1010 X 0111?

- 27) What is the binary product of $1111_2 \times 0101_2$?
- 28) What is the product of $1101_2 \times 2_{10}$ (in binary)?
- 29) What is the product of $1010_2 \times 3_{10}$ (in binary)?
- 30) The 1s complement number 0101 represents _____ in decimal.
- 31) The 1s complement number 1011 represents _____ in decimal.
- 32) The decimal 13 equals _____ (4 bits) in 1s complement.
- 33) The decimal 3 equals _____ (4 bits) in 1s complement.
- 34) When microprocessors process both positive and negative numbers, _____ representation are used.
- 35) The 2s complement number 0101 represents a positive _____ in decimal.
- 36) The 2s complement number 1111 represents a negative _____ in decimal.
- 37) In 2s complement, the MSB is called the _____ bit.
- 38) The decimal -3 equals _____ (4 bits) in 2s complement.
- 39) The decimal 6 equals _____ (4 bits) in 2s complement.
- 40) The decimal -2 equals _____ (4 bits) in 2s complement.
- 41) The sum of the 2s complement numbers 1011 & 1110 equals _____ (4 bits) in 2s complement.
- 42) Subtract 2s complement numbers 0011 from 2s complement numbers 1011 (Give answer in 2s complement).
- 43) Subtract 2s complement numbers 0011 from 2s complement numbers 0111 (Give answer in 2s complement).
- 44) A five bit adder requires _____ half adder(s) and _____ full adder(s).
- 45) A seven bit subtractor requires _____ half subtractor(s) and _____ full subtractor(s).
- 46) A five bit parallel adder/subtractor requires _____ half adder(s), _____ full adder(s), _____ half subtractor(s) and _____ full subtractor(s).