




Chapter 8 - Counters

Ripple Up Counters

0-15				
	D	C	B	A
0				
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				

Ripple Counters use the _____ Flip Flop.

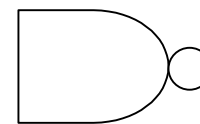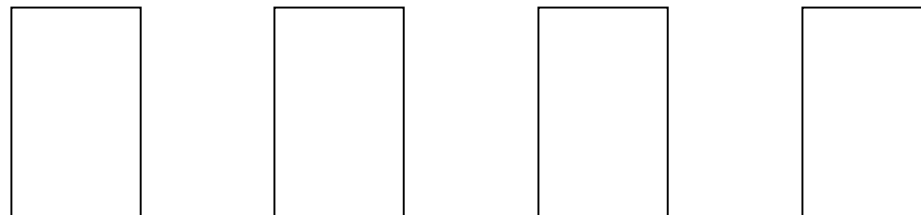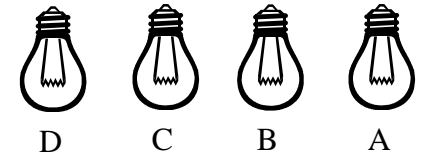The asynchronous and synchronous inputs all stay at a logical _____ for the counter to operate.



4-bit Wave Table for a Mod-16 Counter

