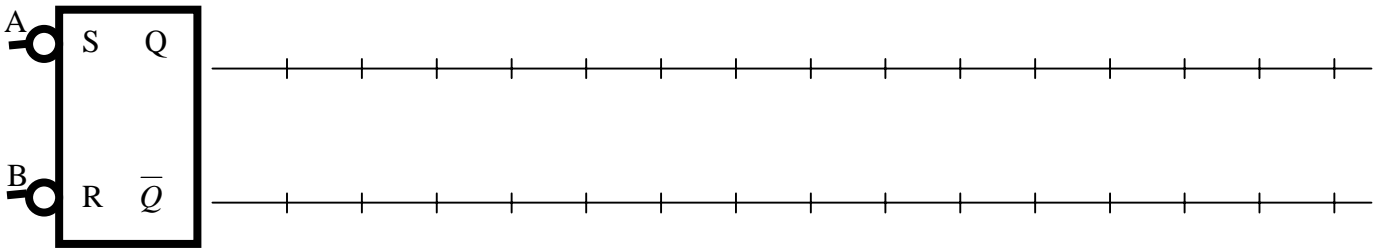
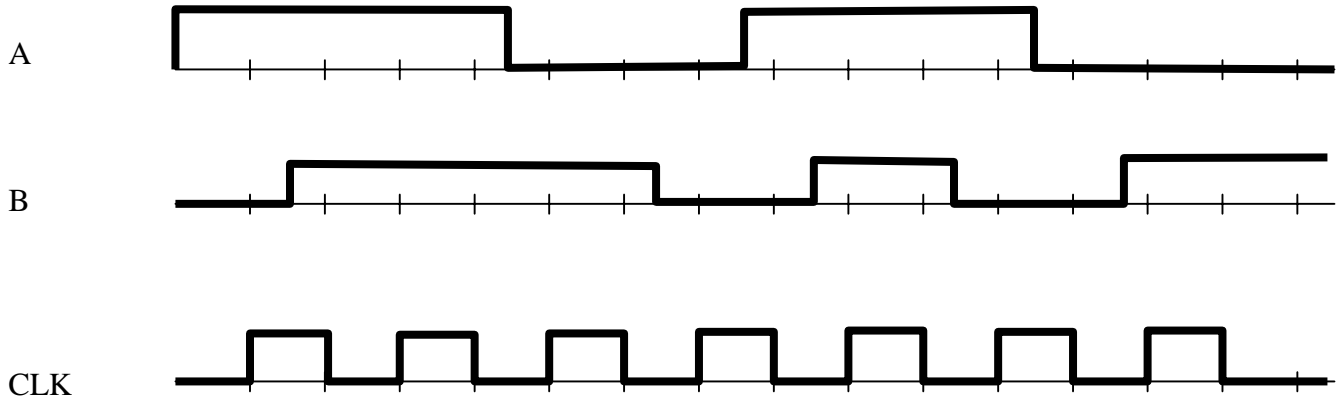

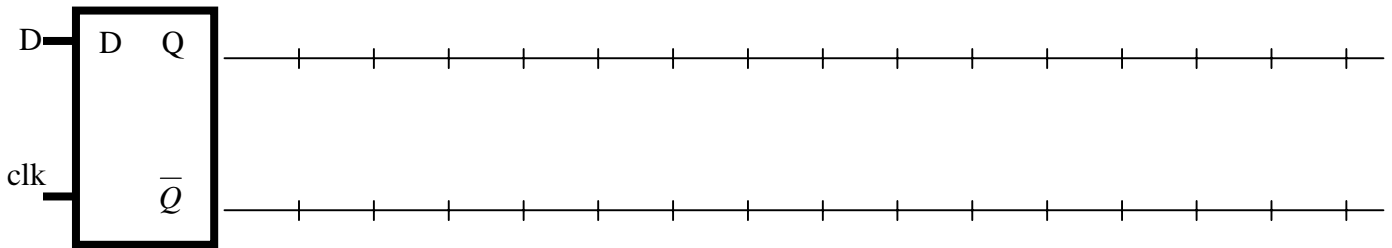
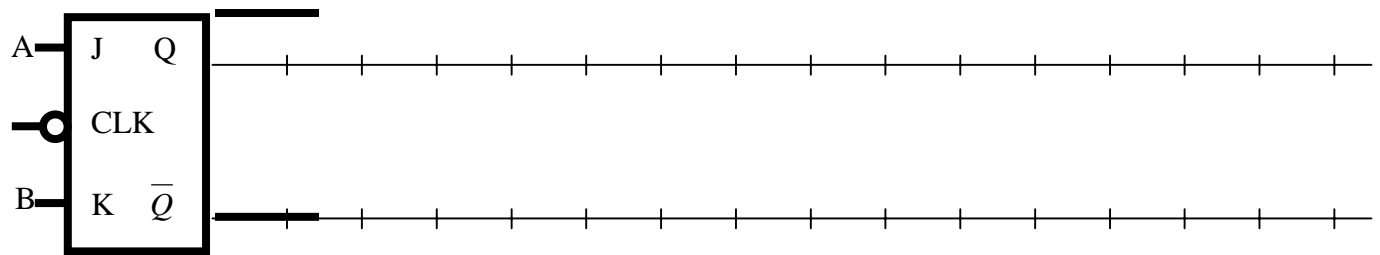



Name _____

JK - RS - D FlipFlops Wave Form Diagrams



assume starts here 



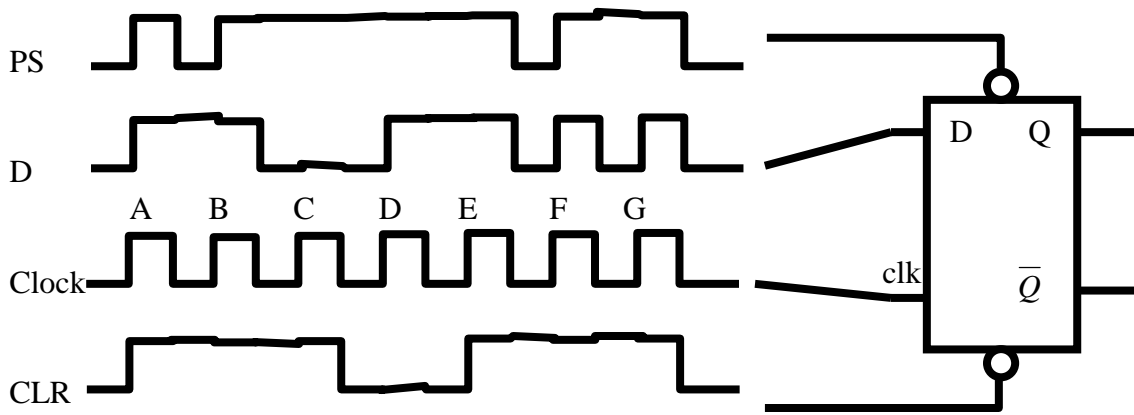

For each pulse of the clock give the logical value (0 or 1) of both Q and \bar{Q} . Also state the mode of operation.

Pulse	Q	\bar{Q}	Mode
A			
B			
C			
D			
E			
F			
G			

Complete the truth table for the following logic symbol.

Mode of Operation	INPUTS					OUTPUTS	
	Asynchronous		Synchronous			Q	\bar{Q}
	PS	CLR	CLK	J	K		