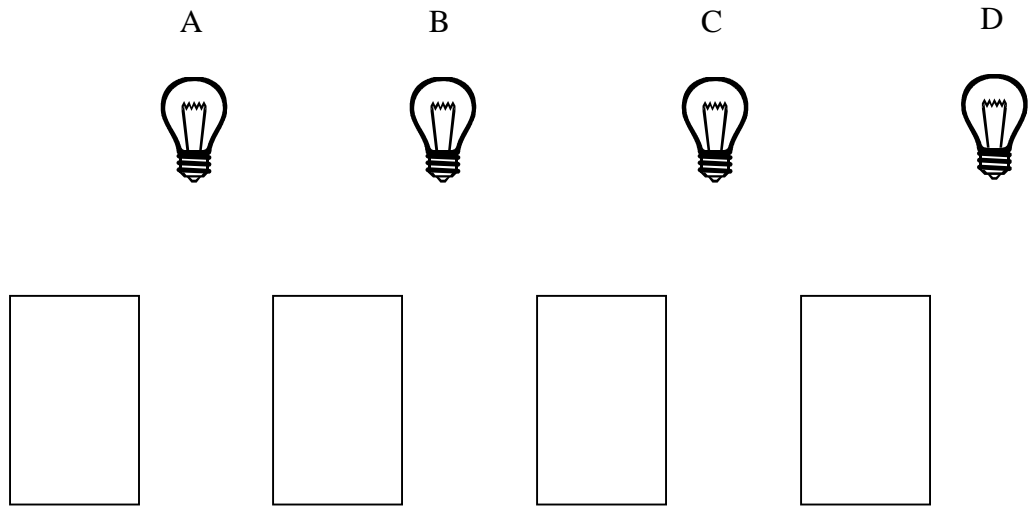
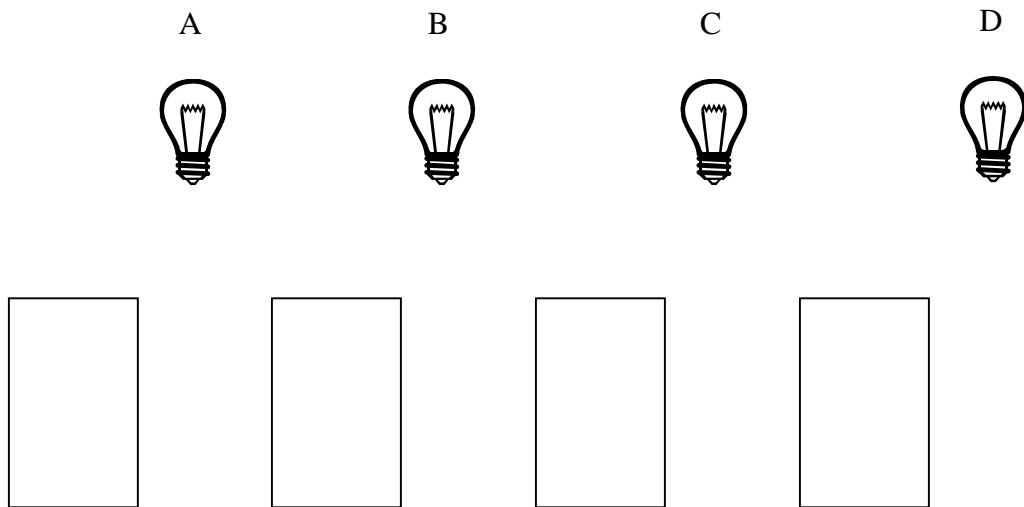


4-bit serial load shift register using (7474) D-Flip Flops



4-bit parallel load recirculating shift register using (7476) J-K Flip Flops



74194 IC wired as a 4-bit serial load shift-right register

