

Name \_\_\_\_\_

Logic Gates  
Homework 4

Draw the logic diagram for the following expressions:


A)  $BA \oplus \overline{BC}$

B)  $(D \oplus EF)D$


C)  $\overline{AC + BC} \oplus AB$

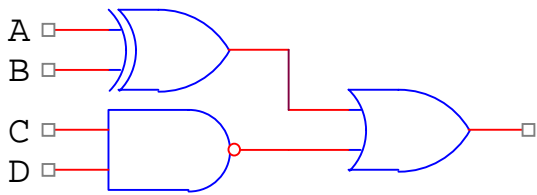D)  $\overline{B \oplus C} \overline{A \oplus D}$

Write the boolean expression for the following logic diagrams:




Boolean Expression: \_\_\_\_\_

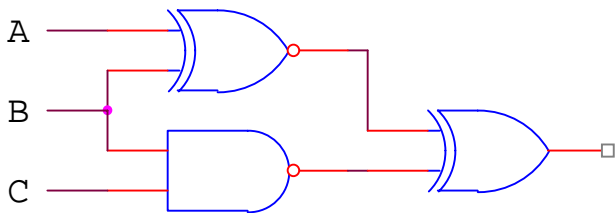


Boolean Expression: \_\_\_\_\_

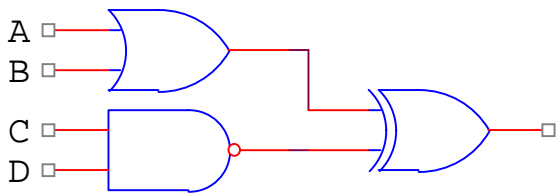Write the boolean expression and complete the truth table for the following logic diagrams:



Boolean Expression: \_\_\_\_\_

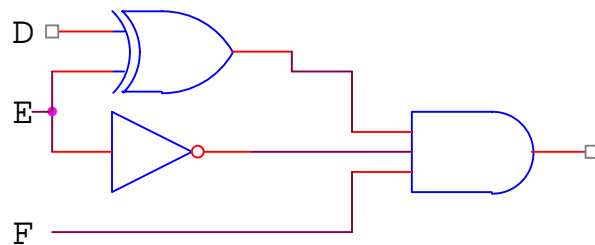

Boolean Expression: \_\_\_\_\_

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
...			

D	E	F
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1