

ICT Logic Gate Pretest

Draw the logic diagram of the following boolean expressions (be neat and use a template):


1. $(A + B)(C + D) = Y$

2. $\overline{N \cdot X} + (A \cdot B) = Y$


3. $(\overline{C} \cdot \overline{W} \cdot \overline{P}) + (V + W) = Y$

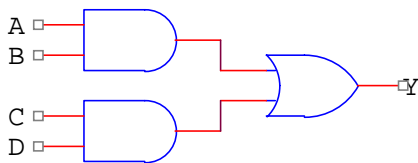4. $\overline{\overline{(A \oplus B)} + (C \cdot D)} = L$


Write the boolean expression for each of the following logic diagrams:




Y = _____

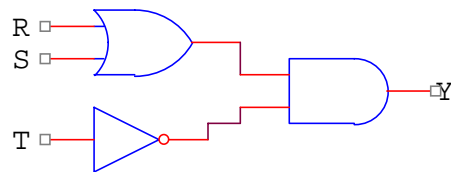

Y = _____

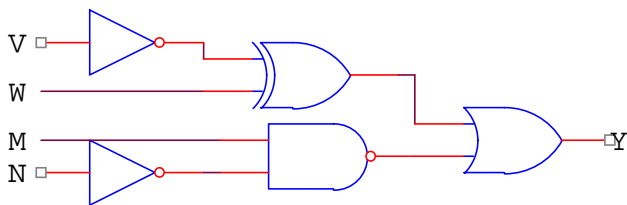

Y = _____

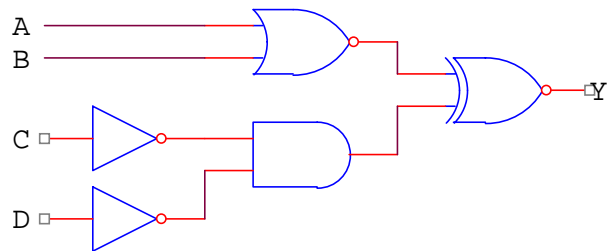

Y = _____

- 9) A NOR gate can be constructed by inverting a(n) _____ gate.
- 10) A XNOR gate can be constructed by inverting a(n) _____ gate.
- 11) LED is an acronym for _____ .


- 12) DIP is an acronym for _____ .
- 13) RAM is an acronym for _____ .
- 14) ROM is an acronym for _____ .
- 15) IC is an acronym for _____ .
- 16) A _____ gate has a unique output of low (or 0) when both inputs are high (or 1).
- 17) A _____ gate has a unique output of low (or 0) when both inputs are low (or 0).
- 18) A NOR gate has a unique output of _____ when both inputs are _____ .
- 19) The _____ and _____ gates have no unique outputs.

For questions 20-22 choose from the following gates (AND, OR, XOR, NAND, NOT)


- 20) The "either but not both gate" is the _____ gate.
- 21) The "all or nothing gate" is the _____ gate.
- 22) The "any or all gate" is the _____ gate.
- 23) Complete the following truth table:


A	B	$A \oplus B$	\overline{AB}	AB	A + B
0	0				
0	1				
1	0				
1	1				

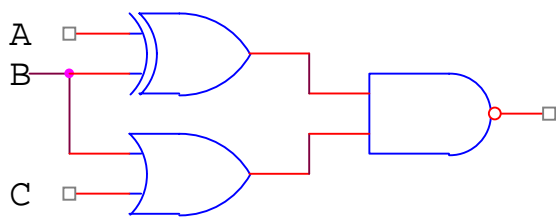24) Complete the truth table for the following:




25) Label the legs of this IC.

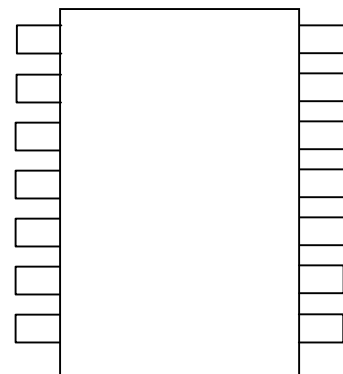

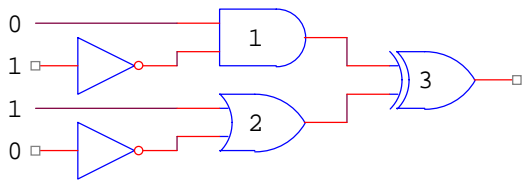

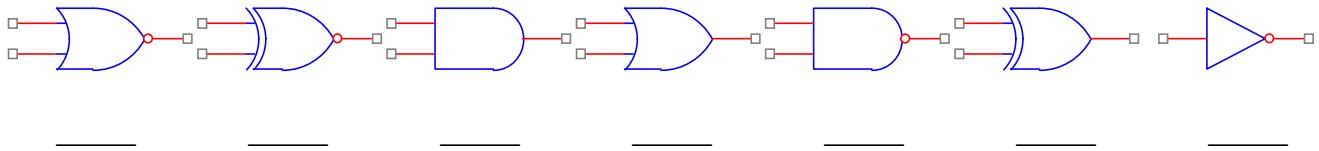- 26) The output of gate 1 is _____.
- 27) The output of gate 2 is _____.
- 28) The output of gate 3 is _____.
- 29) A NOR gate performs the logic function _____.
- a) $A + B$ b) $\overline{A + B}$ c) \overline{AB} d) $\overline{A} \overline{B}$ e) $A \oplus B$
- 30) A NAND gate performs the logic function _____.
- a) $A + B$ b) $\overline{A + B}$ c) \overline{AB} d) $\overline{A} \overline{B}$ e) $A \oplus B$

Name each of the following gates (choose from: NOT, OR, XNOR, XOR, NAND, AND, NOR)



Simplify the following bit-wise expressions:

- 31) $10101 \bullet 11011 \oplus 10011 =$
- 32) $11000 + 10101 \bullet 01010 =$
- 33) $\overline{00110 \oplus 10011} \bullet 11101 + 00100 =$