

Name \_\_\_\_\_

### Logic Gates (Not - And - Or) Wave Form Diagrams

